

# Expressing Flexibility in Logic Synthesis by Boolean Relations

Anna Bernasconi  
Università di Pisa, Italy

- Classic applications
  - Multilevel logic optimization
- Approximate Logic Synthesis
- Bounded-depth logic synthesis via Boolean relations
  - Bi-decomposed Circuits
  - Synthesis with critical signals: P-circuits

# Multilevel logic optimization

Given a multilevel logic network, obtain an **equivalent** representation of the network, **optimal** w.r.t. a cost function involving area and delay

- *identifying subnetworks* to be optimized,
- deriving their *flexibility*
- and *replacing* such subnetworks by *simpler, optimized* ones

## SINGLE-OUTPUT SUBNETWORKS

The **flexibility** for implementing the node's function can be represented by **don't cares**

# Multilevel logic optimization

Given a multilevel logic network, obtain an **equivalent** representation of the network, **optimal** w.r.t. a cost function involving area and delay

- *identifying subnetworks* to be optimized,
- deriving their *flexibility*
- and *replacing* such subnetworks by *simpler, optimized* ones

## SINGLE-OUTPUT SUBNETWORKS

The **flexibility** for implementing the node's function can be represented by **don't cares**

## MULTI-OUTPUT SUBNETWORKS


**Don't cares are not sufficient for representing all the flexibility**

Don't care-based methods allow us to optimize only *one single-output subnetwork at a time*

**Boolean relations describe all the flexibility**

*Boolean relations allow the simultaneous modification of all nodes of a subnetwork*
 
# Minimization of a *two-bit adder* due to the filtering effect of a *comparator* [Brayton, Somenzi, 1989]



$$z = 01 \Rightarrow a + b < 3$$

$$z = 00 \Rightarrow (a + b = 3) \vee (a + b = 4)$$

$$z = 10 \Rightarrow a + b > 4.$$

Input values can be partitioned into three equivalence classes:


Values less than 3: {000, 001, 010}

Values equal to 3 or 4: {011, 100}

Values greater than 4: {101, 110, 111}

The values in each class are not distinguished by the comparator
 
# Minimization of a *two-bit adder* due to the filtering effect of a *comparator* [Brayton, Somenzi, 1989]



$$z = 01 \Rightarrow a + b < 3$$

$$z = 00 \Rightarrow (a + b = 3) \vee (a + b = 4)$$

$$z = 10 \Rightarrow a + b > 4.$$

Input values can be partitioned into three equivalence classes:

Values less than 3: {000, 001, 010}

Values equal to 3 or 4: {011, 100}

Values greater than 4: {101, 110, 111}

The values in each class are not distinguished by the comparator

We can change the output value of the adder, to any other value in the same equivalence class.

## Boolean relation describing the flexible adder

$a_1 \ a_0 \ b_1 \ b_0$	$x_2 \ x_1 \ x_0$
{0000, 0001, 0010, 0100, 1000, 0101}	{000, 001, 010}
{0011, 0110, 1001, 1010, 1100, 0111, 1101}	{011, 100}
{1011, 1110, 1111}	{101, 110, 111}

# Minimization of a *two-bit adder* due to the filtering effect of a *comparator* [Brayton, Somenzi, 1989]

## Minimization with don't cares

including the normal adder as an acceptable implementation

$a_1 a_0 b_1 b_0$	$x_2 x_1 x_0$
1 1 - 0	0 1 1
- 1 1 0	0 1 1
1 0 - 1	0 1 1
- 0 1 1	0 1 1
- 1 1 1	1 0 0
1 1 - 1	1 0 0
1 1 1 -	0 1 0
1 - 1 -	1 0 0

## Minimization of the Boolean relation

much simpler minimum solution

$a_1 a_0 b_1 b_0$	$x_2 x_1 x_0$
0 - 1 -	0 1 0
1 - 0 -	0 1 0
1 - 1 -	1 0 0
- - - 1	0 0 1
- 1 - -	0 0 1

# Approximate Logic Synthesis (ALS)

- Exploit error tolerance of applications to implement approximate designs with
  - smaller area
  - smaller delay
  - or lower energy consumption
- Modify some outputs of a function, so that the produced error is tolerable



# Approximate Logic Synthesis (ALS)

- Exploit error tolerance of applications to implement approximate designs with
  - smaller area
  - smaller delay
  - or lower energy consumption
- Modify some outputs of a function, so that the produced error is tolerable

## ERROR FREQUENCY

number of minterms on which an error occurs, as a fraction of the total number of minterms

## ERROR MAGNITUDE

maximum amount by which the numerical value at the outputs of a function can deviate from the exact value

# ALS and Boolean Relations

[Miao, Gerstlauer, Orshansky, 2013]:

- ALS under arbitrary *error magnitude* and *error frequency* constraints
- Two-level logic minimization algorithm, two-phase approach:
  - 1 derive the solution of the problem constrained only by the *magnitude of errors*
  - 2 the solution is iteratively refined to meet the original *error frequency constraint*

# ALS and Boolean Relations

[Miao, Gerstlauer, Orshansky, 2013]:

- ALS under arbitrary *error magnitude* and *error frequency* constraints
- Two-level logic minimization algorithm, two-phase approach:
  - 1 derive the solution of the problem constrained only by the *magnitude of errors* → expressed and solved using Boolean relations
  - 2 the solution is iteratively refined to meet the original *error frequency constraint*

# ALS constrained by Error Magnitude only

- Multi-output function  $f : \{0, 1\}^n \rightarrow \{0, 1\}^k$
- $M$ : constrain on the magnitude of possible errors

## PROBLEM

Find  $f' : \{0, 1\}^n \rightarrow \{0, 1\}^k$  of **minimal cost** s.t.

$$\forall x \in \{0, 1\}^n \quad |f(x) - f'(x)| \leq M$$

# ALS constrained by Error Magnitude only

- Multi-output function  $f : \{0, 1\}^n \rightarrow \{0, 1\}^k$
- $M$ : constrain on the magnitude of possible errors

## PROBLEM

Find  $f' : \{0, 1\}^n \rightarrow \{0, 1\}^k$  of **minimal cost** s.t.

$$\forall x \in \{0, 1\}^n \quad |f(x) - f'(x)| \leq M$$

- $\forall x \in \{0, 1\}^n$ ,  $e(x)$  = output error set for  $x$   
*additional values that the function can take while satisfying the error magnitude constraint*

$$\mathcal{R}_{f'}(x) \in \{f(x) \cup e(x)\}$$

*each input corresponds to more than one output:  $f'$  becomes a Boolean relation  $\mathcal{R}_{f'}$*

⇒ **minimize the Boolean relation  $\mathcal{R}_{f'}$** , under a given metric (i.e., the number of literals in a SOP representation)

# Example

## ADDER

$x_1 \ x_2$	$f(x_1, x_2)$
00	00
01	01
10	01
11	10

$$L(f) = 6$$

$$SOP(f^{(1)}) = x_1 x_2$$

$$SOP(f^{(2)}) = \bar{x}_1 x_2 + x_1 \bar{x}_2$$

# Example

## ADDER

$x_1 x_2$	$f(x_1, x_2)$
00	00
01	01
10	01
11	10

$$L(f) = 6$$

$$SOP(f^{(1)}) = x_1 x_2$$

$$SOP(f^{(2)}) = \bar{x}_1 x_2 + x_1 \bar{x}_2$$

## ADDER, $M = 1$

$x_1 x_2$	$\mathcal{R}_{f'}(x_1, x_2)$
00	{00, 01}
01	{01, 00, 10}
10	{01, 00, 10}
11	{10, 01, 11}

# Example

## ADDER

$x_1 \ x_2$	$f(x_1, x_2)$
00	00
01	01
10	01
11	10

$$L(f) = 6$$

$$SOP(f^{(1)}) = x_1 x_2$$

$$SOP(f^{(2)}) = \bar{x}_1 x_2 + x_1 \bar{x}_2$$

## ADDER, $M = 1$

$x_1 \ x_2$	$\mathcal{R}_{f'}(x_1, x_2)$
00	{00, 01}
01	{01, 00, 10}
10	{01, 00, 10}
11	{10, 01, 11}

$$L(f') = 0$$

$$SOP(f^{(1)}) = 0$$

$$SOP(f^{(2)}) = 1$$



# Example

## ADDER

$x_1 \ x_2$	$f(x_1, x_2)$
00	00
01	01
10	01
11	10

$$L(f) = 6$$

$$SOP(f^{(1)}) = x_1 x_2$$

$$SOP(f^{(2)}) = \bar{x}_1 x_2 + x_1 \bar{x}_2$$

## ADDER, $M = 1$

$x_1 \ x_2$	$\mathcal{R}_{f'}(x_1, x_2)$	
00	{00, 01}	✗
01	{01, 00, 10}	
10	{01, 00, 10}	
11	{10, 01, 11}	✗

$$L(f') = 0$$

$$SOP(f^{(1)}) = 0$$

$$SOP(f^{(2)}) = 1$$

ERROR FREQUENCY: 50 %

# Frequency constrained ALS algorithm

- The BR solution may not satisfy the **constrain on error frequency**
- Iterative and greedy algorithm for **systematically corrects the wrong outputs** (leading to the smallest cost increase) **until the error frequency constraint is met**

# Frequency constrained ALS algorithm

- The BR solution may not satisfy the **constrain on error frequency**
- Iterative and greedy algorithm for **systematically corrects the wrong outputs** (leading to the smallest cost increase) **until the error frequency constraint is met**

ERROR FREQUENCY: 25 %

$x_1 x_2$	$f(x_1, x_2)$	$\mathcal{R}_{f'}(x_1, x_2)$
00	00	{00, 01} X
01	01	{01, 00, 10}
10	01	{01, 00, 10}
11	10	{10, 01, 11} X

# Frequency constrained ALS algorithm

- The BR solution may not satisfy the **constrain on error frequency**
- Iterative and greedy algorithm for **systematically corrects the wrong outputs** (leading to the smallest cost increase) **until the error frequency constraint is met**

ERROR FREQUENCY: 25 %

$x_1 x_2$	$f(x_1, x_2)$	$\mathcal{R}_{f'}(x_1, x_2)$
00	00	{00, 01}
01	01	{01, 00, 10}
10	01	{01, 00, 10}
11	10	{10, 01, 11} <b>X</b>

$$L(f') = 2$$

$$SOP(f^{(1)}) = 0$$

$$SOP(f^{(2)}) = x_1 + x_2$$

# Bounded-depth logic synthesis via Boolean relations: Bi-Decomposition (joint work with R. K. Brayton, V. Ciriani, G. Trucco, and T. Villa)

$$f : \{0, 1\}^n \rightarrow \{0, 1, -\}$$

$f = (f_{on}, f_{dc}, f_{off})$  can be covered with

- a SOP derived by the on-set (+ some dc-points)
- a POS resulting from the complement of a SOP for the off-set (+ some dc-points)
- ★ *Which one gives the best cover, the SOP or the POS form?*
- ★ *Can we study a form that is part in SOP and part in POS form, and is better than both?*

# Bounded-depth logic synthesis via Boolean relations: Bi-Decomposition (joint work with R. K. Brayton, V. Ciriani, G. Trucco, and T. Villa)

$$f : \{0, 1\}^n \rightarrow \{0, 1, -\}$$

$f = (f_{on}, f_{dc}, f_{off})$  can be covered with

- a SOP derived by the on-set (+ some dc-points)
- a POS resulting from the complement of a SOP for the off-set (+ some dc-points)
- ★ *Which one gives the best cover, the SOP or the POS form?*
- ★ *Can we study a form that is part in SOP and part in POS form, and is better than both?*

We propose a **bi-decomposed form** that is part in SOP form and part in POS

$$f_B = \overline{f_0} \text{ op } f_1$$

# Bounded-depth logic synthesis via Boolean relations: Bi-Decomposition

$x_3x_4 \backslash x_1x_2$	00	01	11	10
00	0	1	1	1
01	0	0	0	0
11	0	1	1	1
10	1	1	1	1

(a)  $f$

$x_3x_4 \backslash x_1x_2$	00	01	11	10
00	0	1	1	1
01	0	0	0	0
11	0	1	1	1
10	1	1	1	1

(b) SOP for  $f$

$x_3x_4 \backslash x_1x_2$	00	01	11	10
00	0	1	1	1
01	0	0	0	0
11	0	1	1	1
10	1	1	1	1

(c) POS for  $f$

$x_3x_4 \backslash x_1x_2$	00	01	11	10
00	0	1	1	1
01	0	0	0	0
11	0	1	1	1
10	1	1	1	1

(d) Bi-cond. form for  $f$

- $f_{SOP} = f_1^{SOP} = x_1\bar{x}_2 + x_1x_3 + x_1x_4 + \bar{x}_2x_3 + \bar{x}_2x_4$  10 literals
- $f_{POS} = \bar{f}_0^{POS} = (x_1 + \bar{x}_2)(x_1 + x_3 + x_4)(\bar{x}_2 + x_3 + x_4)$  8 literals

# Bounded-depth logic synthesis via Boolean relations: Bi-Decomposition

$x_3 \backslash x_1 x_2$	00	01	11	10
00	0	1	1	1
01	0	0	0	0
11	0	1	1	1
10	1	1	1	1

(a) f

$x_3 \backslash x_1 x_2$	00	01	11	10
00	0	1	1	1
01	0	0	0	0
11	0	1	1	1
10	1	1	1	1

(b) SOP for f

$x_3 \backslash x_1 x_2$	00	01	11	10
00	0	1	1	1
01	0	0	0	0
11	0	1	1	1
10	1	1	1	1

(c) POS for f

$x_3 \backslash x_1 x_2$	00	01	11	10
00	0	1	1	1
01	0	0	0	0
11	0	1	1	1
10	1	1	1	1

(d) Bi-cond. form for f

- $f_{SOP} = f_1^{SOP} = x_1 \bar{x}_2 + x_1 x_3 + x_1 x_4 + \bar{x}_2 x_3 + \bar{x}_2 x_4$  10 literals
- $f_{POS} = \bar{f}_0^{POS} = (x_1 + \bar{x}_2)(x_1 + x_3 + x_4)(\bar{x}_2 + x_3 + x_4)$  8 literals
- $f_B = \bar{f}_0 + f_1 = ((x_1 + \bar{x}_2)(x_3 + x_4)) + x_1 \bar{x}_2$  6 literals

1000 is in the the OFF set of  $\bar{f}_0$  and in the ON set of  $f_1$   
thus is in the ON set of the  $\bar{f}_0 + f_1$



# Synthesis of Bi-decomposed Circuits and Boolean relations

$f : \{0, 1\}^n \rightarrow \{0, 1, -\},$

$f = u \text{ op } v$

$u \leftarrow \overline{f_0}, v \leftarrow f_1$

**Inputs** of  $u$  and  $v$ : the same as the inputs of  $f$ :  $x_1, \dots, x_n$

**Output:** is the output that **op** takes on  $u(x_1, \dots, x_n)$  and  $v(x_1, \dots, x_n)$

# Synthesis of Bi-decomposed Circuits and Boolean relations

$$f : \{0, 1\}^n \rightarrow \{0, 1, -\},$$

$$f = u \text{ op } v$$

$$u \leftarrow \overline{f_0}, v \leftarrow f_1$$

**Inputs** of  $u$  and  $v$ : the same as the inputs of  $f$ :  $x_1, \dots, x_n$

**Output**: is the output that **op** takes on  $u(x_1, \dots, x_n)$  and  $v(x_1, \dots, x_n)$

## AND GROUP

$u v$	AND
$\overline{u} v$	$\neq$
$u \overline{v}$	$\neq$
$\overline{u} \overline{v}$	NOR

## OR GROUP

$u + v$	OR
$\overline{u} + v$	$\Rightarrow$
$u + \overline{v}$	$\Leftarrow$
$\overline{u} + \overline{v}$	NAND

## XOR GROUP

$u \oplus v$	XOR
$u \overline{\oplus} v$	XNOR

# Synthesis of Bi-decomposed Circuits and Boolean relations

$$f : \{0, 1\}^n \rightarrow \{0, 1, -\},$$

$$f = u \text{ op } v$$

$$u \leftarrow \overline{f_0}, v \leftarrow f_1$$

**Inputs** of  $u$  and  $v$ : the same as the inputs of  $f$ :  $x_1, \dots, x_n$

**Output**: is the output that **op** takes on  $u(x_1, \dots, x_n)$  and  $v(x_1, \dots, x_n)$

## AND GROUP

$uv$	AND
$\overline{u}v$	$\neq$
$u\overline{v}$	$\neq$
$\overline{u}\overline{v}$	NOR

## OR GROUP


$u+v$	OR
$\overline{u}+v$	$\Rightarrow$
$u+\overline{v}$	$\Leftarrow$
$\overline{u}+\overline{v}$	NAND

## XOR GROUP

$u \oplus v$	XOR
$u \overline{\oplus} v$	XNOR

- The two-input operator induces flexibility that cannot be expressed exactly by don't care conditions only: **a Boolean relation is required**
- For each binary **op**, we define  $\mathcal{R}_{op} : \{0, 1\}^n \rightarrow \{0, 1\}^2$  s.t.
  - the set of **functions compatible with  $\mathcal{R}_{op}$**  corresponds to the set of pairs  $(u, v)$  occurring in all **bi-decomposed circuit implementations of  $f$**  w.r.t. **op**.
  - an **optimal solution of  $\mathcal{R}_{op}$**  is an **optimal bi-decomposed circuit** for  $f$

# Construction of $\mathcal{R}_{OR}$

 

- $\forall x \in f_{on}, x$  must be associated to one of the three output values on which  $u + v$  evaluates to 1

$$\mathcal{R}_{OR}(x) = \{01, 10, 11\} = \{1-, -1\}$$

- $\forall x \in f_{off}, x$  must be associated to the output **00** on which  $u + v$  evaluates to 0

$$\mathcal{R}_{OR}(x) = 00$$

- $\forall x \in f_{dc}, x$  can be associated to any output

$$\mathcal{R}_{OR}(x) = \{--\}$$

# Construction of $\mathcal{R}_{op}$

## AND table

	$\mathcal{R}_{AND}$	$\mathcal{R}_{\neq}$	$\mathcal{R}_{NOR}$	$\mathcal{R}_{\neq}$
$x \in f_{on}$	$\{11\}$	$\{01\}$	$\{00\}$	$\{10\}$
$x \in f_{off}$	$\{0-, -0\}$	$\{1-, -0\}$	$\{1-, -1\}$	$\{0-, -1\}$
$x \in f_{dc}$	$\{--\}$	$\{--\}$	$\{--\}$	$\{--\}$

## OR table

	$\mathcal{R}_{OR}$	$\mathcal{R}_{\Rightarrow}$	$\mathcal{R}_{NAND}$	$\mathcal{R}_{\Leftarrow}$
$x \in f_{on}$	$\{1-, -1\}$	$\{0-, -1\}$	$\{0-, -0\}$	$\{1-, -0\}$
$x \in f_{off}$	$\{00\}$	$\{10\}$	$\{11\}$	$\{01\}$
$x \in f_{dc}$	$\{--\}$	$\{--\}$	$\{--\}$	$\{--\}$

## XOR table

	$\mathcal{R}_{XNOR}$	$\mathcal{R}_{XOR}$
$x \in f_{on}$	$\{00, 11\}$	$\{01, 10\}$
$x \in f_{off}$	$\{01, 10\}$	$\{00, 11\}$
$x \in f_{dc}$	$\{--\}$	$\{--\}$

# Construction of $\mathcal{R}_{op}$

The three tables are distinguished by whether

- the **offset** is partitioned (**AND group**)
- the **onset** is partitioned (**OR group**)
- or **both** are partitioned (**XOR group**)

How this partitioning is done is task of the *Boolean relation minimizer*

# Construction of $\mathcal{R}_{op}$

The three tables are distinguished by whether

- the **offset** is partitioned (**AND group**)
- the **onset** is partitioned (**OR group**)
- or **both** are partitioned (**XOR group**)

How this partitioning is done is task of the *Boolean relation minimizer*

Bi-decomposed circuit minimization problem  
 $\iff$   
problem of finding an optimal implementation of  $\mathcal{R}_{op}$

Good gains in a majority of benchmarks against affordable increases in synthesis time

# Synthesis with critical signals: P-circuits

(joint work with V. Ciriani, G. Trucco, and T. Villa)

## Scenario

- Logic synthesis in presence of critical signals that should be moved toward the output
- signals with **high switching** activity  
→ for decreasing power consumption
- **late arriving** signals  
→ for decreasing circuit delay



# Synthesis with critical signals: P-circuits

(joint work with V. Ciriani, G. Trucco, and T. Villa)

## Scenario

- Logic synthesis in presence of critical signals that should be moved toward the output
- signals with **high switching** activity
  - for decreasing power consumption
- **late arriving** signals
  - for decreasing circuit delay

## PROBLEM

Restructure (or synthesize) a circuit in order to move critical signals near to the output (decreasing the cone of influence)


- **minimizing** the circuit **area**
- keeping the number of levels **bounded**
- performing an **efficient** minimization

# Simple solution: Shannon decomposition

- $x$  is the critical signal


$$f = \bar{x} f_{|x=0} + x f_{|x=1}$$

- the cofactors  $f_{|x=0}$  and  $f_{|x=1}$  do not depend on  $x$
- $x$  is near to the output

 


# Problem of Shannon approach

Let  $x = x_1$

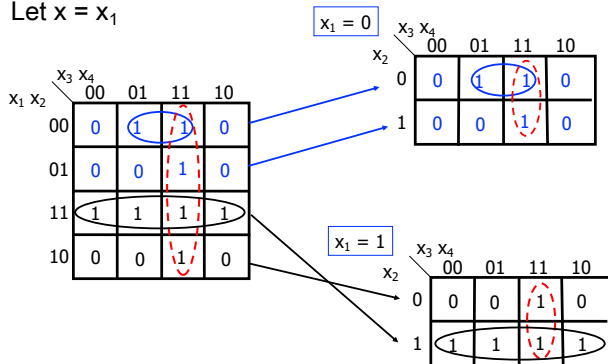

# Problem of Shannon approach

Let  $x = x_1$

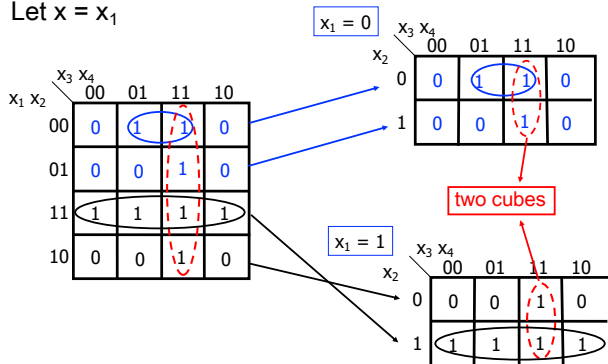

*It is not a compact representation*

# Decomposition with intersection

- try not to split the cubes
- let the critical signal near to the output

## IDEA

- the cubes that **do not depend on  $x$**  and cross the two sets are not projected
- how to identify these cubes?

# Decomposition with intersection

- try not to split the cubes
- let the critical signal near to the output

## IDEA

- the cubes that **do not depend on  $x$**  and cross the two sets are not projected
- how to identify these cubes?

They are in the **intersection between the two cofactors**

$$I = f_{|x_i=0} \cap f_{|x_i=1}$$

- keep  **$I$  unprojected**, and project only the minterms in  $f_{|x_i=0} \setminus I$  and  $f_{|x_i=1} \setminus I$

# Example

		$x_3 \ x_4$			
$x_1 \ x_2$		00	01	11	10
	00	0	1	1	0
	01	0	0	1	0
	11	1	1	1	1
	10	0	0	1	0

$x = x_1$

Intersection

$x_1 = 0$


		$x_3 \ x_4$			
$x_2$		00	01	11	10
	0	0	1	1	0
	1	0	0	1	0

$x_1 = 1$

		$x_3 \ x_4$			
$x_2$		00	01	11	10
	0	0	0	1	0
	1	1	1	1	1


		$x_3 \ x_4$			
$x_2$		00	01	11	10
	0	0	0	1	0
	1	0	0	1	0

# Example

 



# Example

 

# Example

Decomposition with intersection

		$x_3 x_4$			
$x_1$	$x_2$	00	01	11	10
	0	0	1	1	0
	1	0	0	1	0
	11	1	1	1	1
	10	0	0	1	0

The cubes are  
not split

Intersection

$x_1 = 0$

		$x_3 x_4$			
		00	01	11	10
$x_2$	0	0	1	1	0
	1	0	0	0	0

$x_1 = 1$

		$x_3 x_4$			
		00	01	11	10
$x_2$	0	0	0	0	0
	1	1	1	1	1

		$x_3 x_4$			
		00	01	11	10
$x_2$	0	0	0	1	0
	1	0	0	1	0

# P-circuits for completely specified functions

- if a **point is in  $I$**  and is useful for a better minimization of  $f_{|x_i=0}$  and  $f_{|x_i=1}$ , **it can be kept both in the cofactors and in the intersection**
- if a **point is covered in both the projected cofactors**, it is **not necessary to cover it in  $I$**  (replaced by a don't care in  $I$ )

# P-circuits for completely specified functions

- if a **point is in  $I$**  and is useful for a better minimization of  $f|_{x_i=0}$  and  $f|_{x_i=1}$ , **it can be kept both in the cofactors and in the intersection**
- if a **point is covered in both the projected cofactors**, it is **not necessary to cover it in  $I$**  (replaced by a don't care in  $I$ )

## P-CIRCUIT

A *P-circuit* of a completely specified function  $f$  is the circuit

$$P(f) = \bar{x}_i f^= + x_i f^\neq + f^I$$

- ①  $I = f|_{x_i=0} \cap f|_{x_i=1}$
- ②  $(f|_{x_i=0} \setminus I) \subseteq f^= \subseteq f|_{x_i=0}$
- ③  $(f|_{x_i=1} \setminus I) \subseteq f^\neq \subseteq f|_{x_i=1}$
- ④  $\emptyset \subseteq f^I \subseteq I$
- ⑤  $P(f) = f$

# Minimization of P-circuits using Boolean Relation

Find the sets  $f^=, f^\neq, f^l$  leading to a **P-circuit of minimal cost**

- $f : \{0, 1\}^n \rightarrow \{0, 1\}$        $\mathcal{R}_f : \{0, 1\}^{n-1} \rightarrow \{0, 1\}^3$
- **Input set for  $\mathcal{R}_f$** : all input variables but the critical signal  $x_i$
- **Output set for  $\mathcal{R}_f$** : all triple of functions  $f^=, f^\neq, f^l$  defining a P-circuit for  $f$

# Minimization of P-circuits using Boolean Relation

Find the sets  $f^=, f^\neq, f^!$  leading to a **P-circuit of minimal cost**

- $f : \{0, 1\}^n \rightarrow \{0, 1\}$        $\mathcal{R}_f : \{0, 1\}^{n-1} \rightarrow \{0, 1\}^3$
- **Input set for  $\mathcal{R}_f$ :** all input variables but the critical signal  $x_i$
- **Output set for  $\mathcal{R}_f$ :** all triple of functions  $f^=, f^\neq, f^!$  defining a P-circuit for  $f$

$x_1 \dots x_{i-1} x_{i+1} \dots x_n$	$\mathcal{R}_f = (f^=, f^\neq, f^!)$
points in $f _{x_i=0} \setminus I$	$\{100\}$
points in $f _{x_i=1} \setminus I$	$\{010\}$
points in $I$	$\{- - 1, 11-\}$
all other points	$\{000\}$

# Minimization of P-circuits using Boolean Relation

Find the sets  $f^=, f^{\neq}, f^!$  leading to a **P-circuit of minimal cost**

- $f : \{0, 1\}^n \rightarrow \{0, 1\}$        $\mathcal{R}_f : \{0, 1\}^{n-1} \rightarrow \{0, 1\}^3$
- **Input set for  $\mathcal{R}_f$ :** all input variables but the critical signal  $x_i$
- **Output set for  $\mathcal{R}_f$ :** all triple of functions  $f^=, f^{\neq}, f^!$  defining a P-circuit for  $f$

$x_1 \dots x_{i-1} x_{i+1} \dots x_n$	$\mathcal{R}_f = (f^=, f^{\neq}, f^!)$
points in $f _{x_i=0} \setminus I$	$\{100\}$
points in $f _{x_i=1} \setminus I$	$\{010\}$
points in $I$	$\{- - 1, 11-\}$
all other points	$\{000\}$

## THEOREM

**P-circuit** minimization for  $f$   
 $\iff$   
 minimization of the **Boolean relation  $\mathcal{R}_f$**

P-circuits minimized with Boolean relations are more compact than P-circuits expressed and minimized as incompletely specified functions

- **Boolean relations can be extremely useful for modeling Boolean hard optimization problems**
  - with Boolean relations we can model problems that cannot be completely described with incompletely specified functions
- **Problem:** scalability of the approach
  - Boolean relation minimization is a very hard problem
  - Boolean relation minimizers cannot handle relations with many outputs
- Boolean relations have been successfully used in logic synthesis to solve problems that can be cast as the minimization of *relations with a constant number of outputs* (2, 3)



THANK YOU